
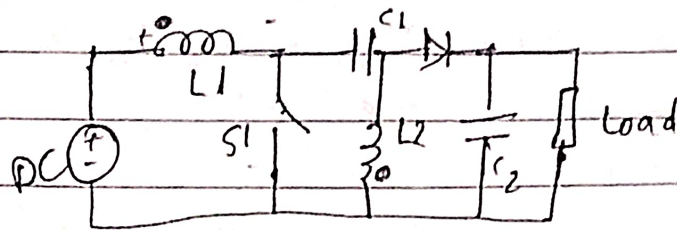


## SEPIC converter

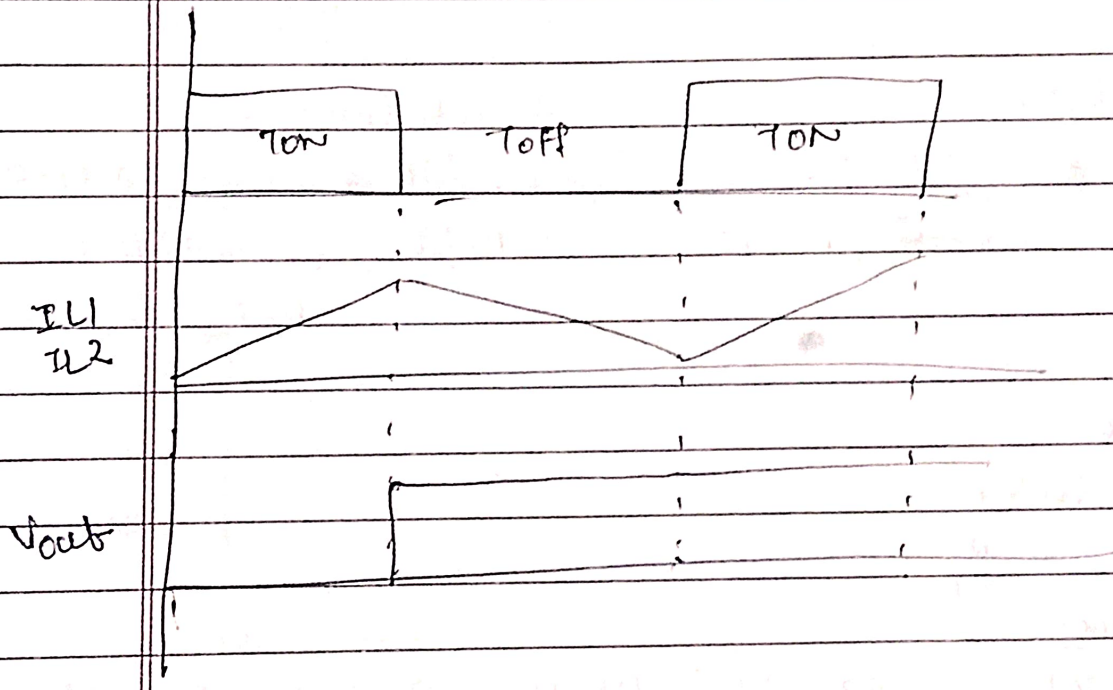


Single ended primary inductance converters


- switching is easier
- non-inverting op





Ton 1

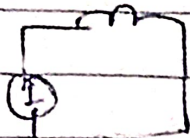

Ton 2

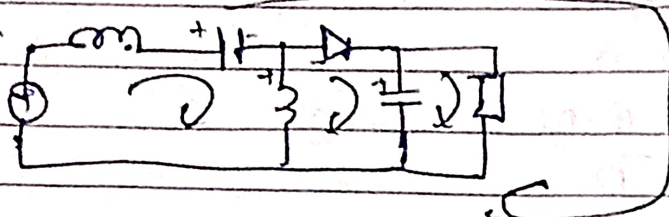

Ton 2

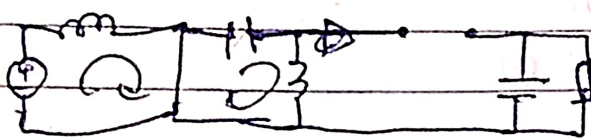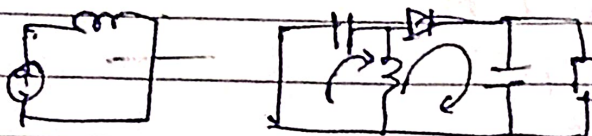

$$f = 20 \text{ kHz}$$

$$V_g = 24 \text{ V}$$

$$D = 0.5$$

$$\Delta I_L = 30\%$$

$$\frac{\Delta V_C}{V} = 2\%$$

$$P_o = 200 \text{ W}$$

### Derivations

1) ON state

$$V_{L1(\text{ON})} = V_g$$

$$V_{L2(\text{ON})} = -V_{C1}$$

$$i_{C1(\text{ON})} = i_{L2}$$

$$i_{C2(\text{ON})} = -i_o$$

2) OFF state

$$V_g = V_{L1(\text{OFF})} + V_{C1} + V_o$$

$$V_{L1(\text{OFF})} = V_g - V_{C1} - V_o$$

$$V_{L2(\text{OFF})} = V_o$$

### Volt-sec Rule

$$\textcircled{1} V_g DT + (V_g - V_{C1} - V_o)(1-D)T = 0$$

$$V_g - V_{C1}(1-D) - V_o(1-D) = 0$$



$$\frac{V_s - V_o(1-D)}{1-D} = V_{C1} \quad \text{--- (1)}$$

$$\textcircled{2} \quad V_{L2(\text{avg})} DT + V_{L2(\text{off})} (1-D)T = 0$$

$$-V_{C1} D + V_o(1-D) = 0$$

$$V_{C1} = \frac{V_o(1-D)}{D} \quad \text{--- (2)}$$

$$\therefore \frac{V_s - V_o(1-D)}{1-D} = \frac{V_o(1-D)}{D}$$

$$\frac{V_s}{1-D} = V_o + \frac{V_o(1-D)}{D}$$

$$\frac{V_s}{1-D} = \frac{V_o D + V_o(1-D)}{D}$$

$$\frac{V_s}{1-D} = \frac{V_o}{D}$$

$$\therefore V_o = \frac{V_s D}{1-D}$$

② Power

$$P_o = P_i$$

$$V_o I_o = V_i I_i$$

$$\frac{V_s D}{1-D} I_o = V_s I_i$$

$$\therefore I_o = I_i \frac{1-D}{D}$$

$$\textcircled{5} \quad i_{C2} = i_o$$

$$\Delta V_{C1} = \frac{1}{C_1} \frac{DT}{1-D}$$

$$\Delta V_{C2} = \frac{i_o DT}{C_2}$$

$$\textcircled{7} \quad V_{L1} = L_1 \frac{\Delta I_{L1}}{DT}$$

$$V_{L1} = V_s$$

$$\Delta I_{L1} = \frac{V_s DT}{L_1}$$

$$\Delta I_{L2} = \frac{V_s DT}{L_2}$$

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

⑥ Critical Inductance

$$I_{L1} - \frac{\Delta I_{L1}}{2} = 0$$

$$I_{L1} = \Delta I_{L1}$$

$$I_{L1} = \frac{V_s D^2 T}{2 L_1}$$

$$i_{L1} = i_s$$

$$L_1 = \frac{V_s}{i_s} \frac{DT}{2}$$

$$L_1 = \frac{V_o}{I_o} \frac{(1-D)^2 T}{2}$$

$$L_1 = R \frac{(1-D)^2 T}{2}$$

$$I_{L2} - \frac{\Delta I_{L2}}{2} = 0$$

$$I_{L2} = \frac{\Delta I_{L2}}{2}$$

$$I_{L2} = \frac{V_s DT}{L_2}$$

$$I_{L2} = I_o$$

$$L_2 = \frac{V_s}{I_o} DT$$

$$L_2 = R \frac{(1-D) T}{2}$$



## Designing a SEPIC.

$$\begin{aligned} V_i &= 24V & f &= 20 \text{ kHz} & \frac{\Delta V_c}{V} &= 2\% \\ D &= 0.5 & \frac{\Delta I_L}{I} &= 30\% & P_i &= 200W \end{aligned}$$

$$1) \quad \therefore V_o = V_s \frac{D}{(1-D)}$$

$$\therefore V_o = V_s = 24V.$$

$$\begin{aligned} 2) \quad P_i &= V_i I_i & D &= 0.5 \\ 200 &= 24 I_i & \text{So } I_o &= I_i \\ I_i &= 8.333A. \end{aligned}$$

$$3) \quad \Delta I_L = \frac{V_{in} D}{L f_s} \quad \text{Since } D=0.5 \quad L_1 = L_2$$

$$L = \frac{V_{in} D}{\Delta I_L f_s}$$

$$= \frac{24 \times 0.5}{0.3 \times 8.33 \times 20 \times 1000}$$

$$= 0.240 \text{ mH}$$

$$\therefore L_1 \geq L_2 \geq 0.240 \text{ mH}$$

$$4) \quad i_c = C_1 \frac{\Delta V_c}{DT}$$

$$i_c = i_o$$

$$C_1 = \frac{DT i_o}{\Delta V_c}$$

$$C_1 = \frac{D \times i_o}{f_s \times \Delta V_c}$$

$$= \frac{0.5 \times 8.333}{20 \times 1000 \times 0.02 \times 24}$$

$$= 0.434027 \text{ mF}$$

$$\therefore C_1 \geq C_2 \geq 0.434027 \text{ mF}$$

$$5) \quad R = ?$$

$$L_1 = R \frac{(1-D)^2}{D} \frac{T}{2}$$

$$R = \frac{0.5 \times 0.240 \times 10^{-3} \times 2 \times 20 \times 1000}{(1-0.5)^2} = 20 \Omega$$